
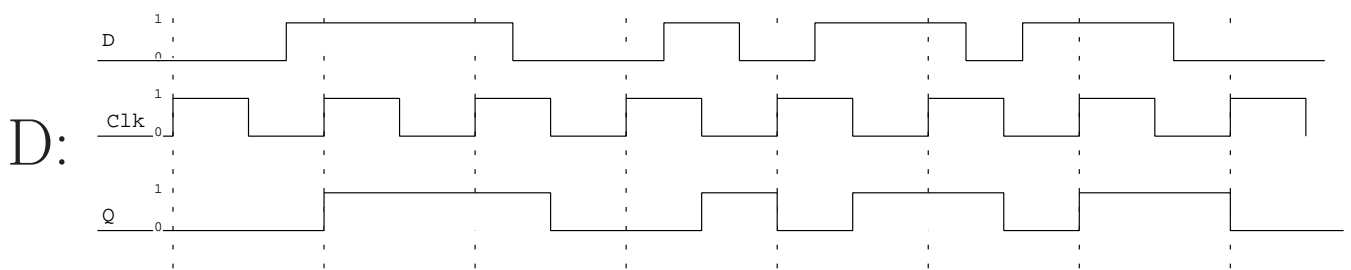
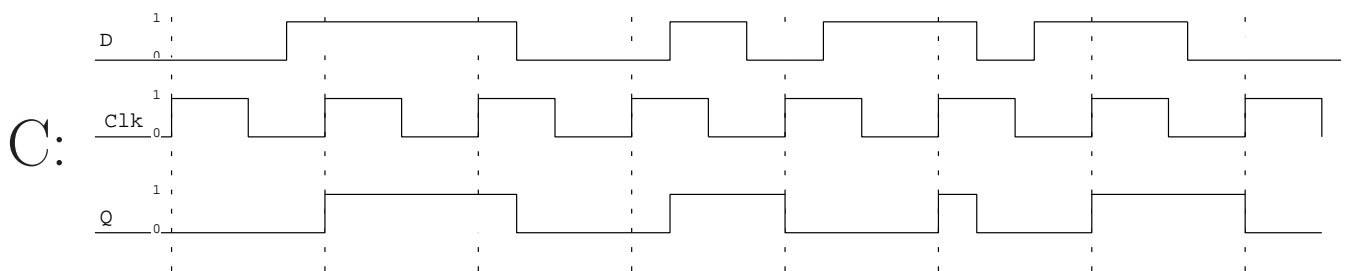
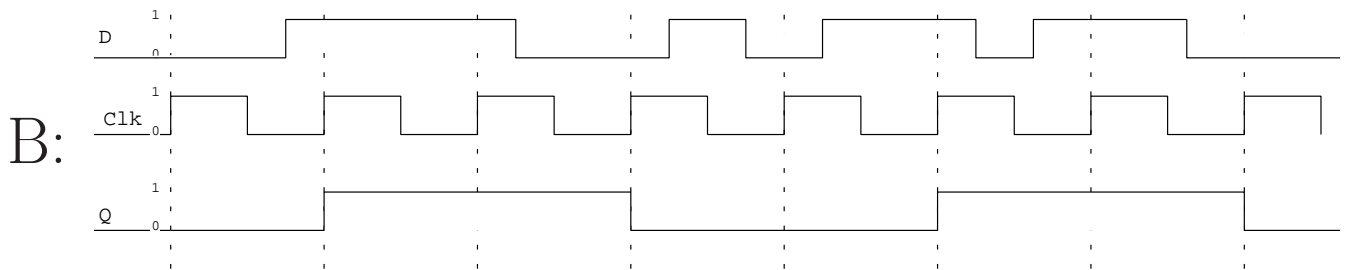


Name: _____

Flip-Flop Behavior

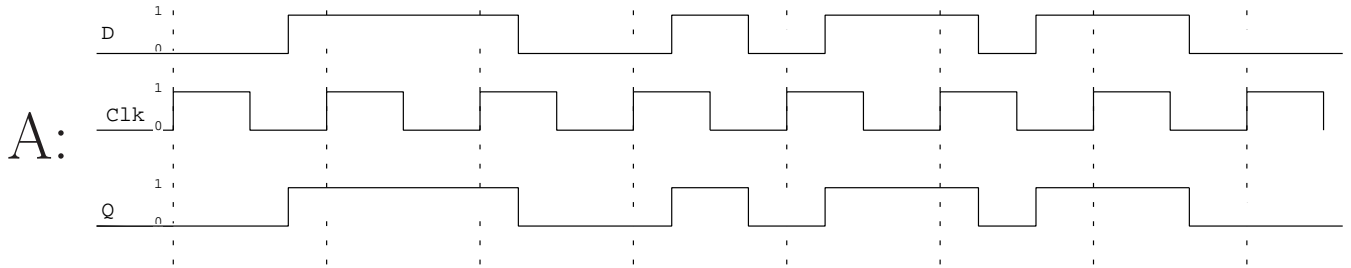Which timing diagram below demonstrates the correct behavior of a *rising-edge* triggered flip-flop?



E: None of the above